

# Analog details behind the digital abstraction

Vikas Dhiman for ECE275



May 9, 2024

Some of the material is out of the textbook. Additional resources include Appendix B of Brown and Vranesic book, “Fundamentals of digital logic.”


## 1 Objectives

1. Describe how tri-state and open-collector outputs are different from totem-pole outputs
2. Compute noise margin of one device driving the same time


## 2 FPGA [1, Section B.6.5]

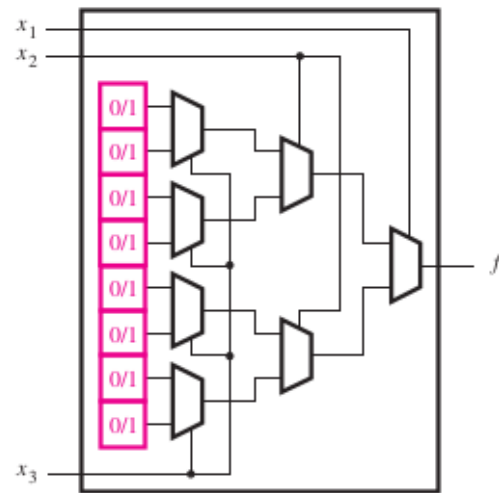 

**Figure B.37** A three-input LUT.

 


**Figure B.38** Inclusion of a flip-flop in an FPGA logic element.

 


**Figure B.39** A section of a programmed FPGA.


**Definition 1** (Random Access Memory (RAM)). *Structure of a RAM is as follows:*

 


**Figure 5.39**  $4 \times 3$  memory array: (a) symbol, (b) function

 

**Figure 5.40** 32 Kb array: depth =  $2^{10} = 1024$  words, width = 32 bits

 


**Figure B.64** An SRAM cell.

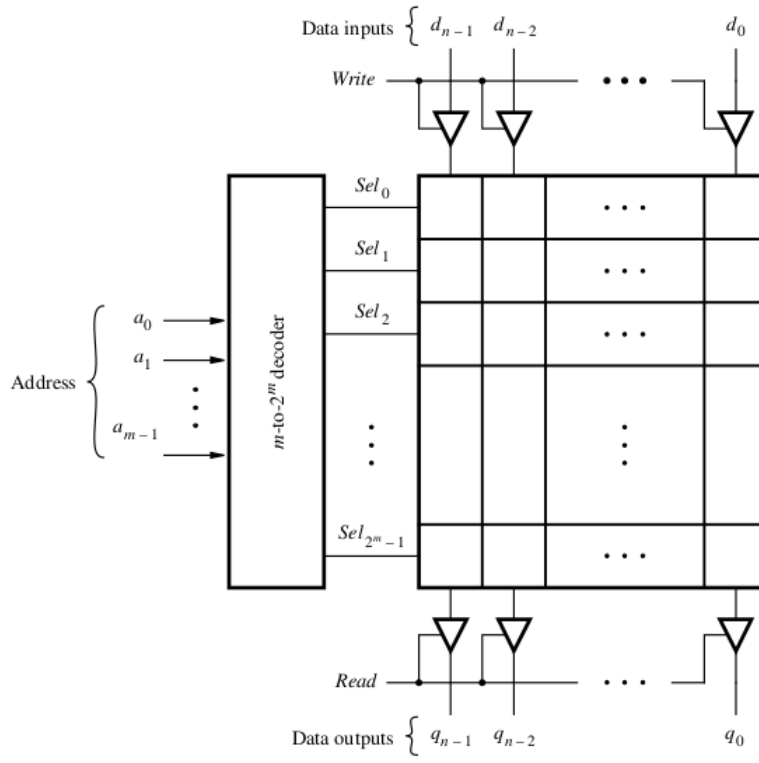

**Figure B.66** A  $2^m \times n$  SRAM block.


**Definition 2** (Read Only Memory (ROM)). *Structure of a ROM is as follows:*

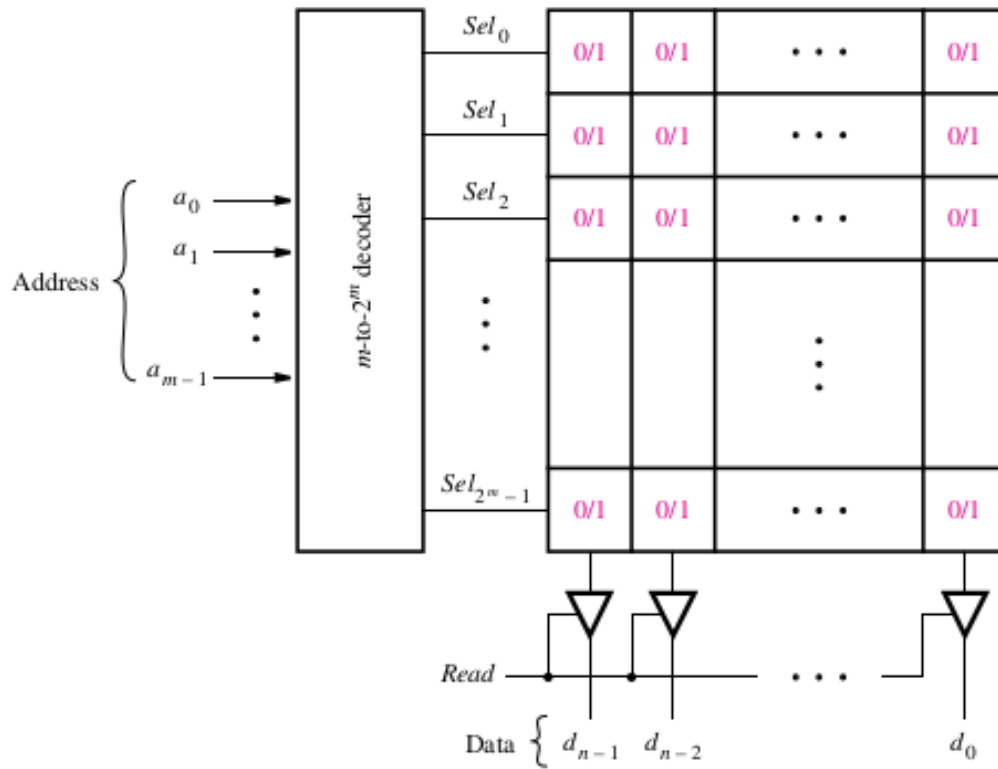

**Figure B.72** A  $2^m \times n$  read-only memory (ROM) block.

**Example 1.** Draw a Multiplexer using sum of products form.

### 3 Logic levels and Noise Margins

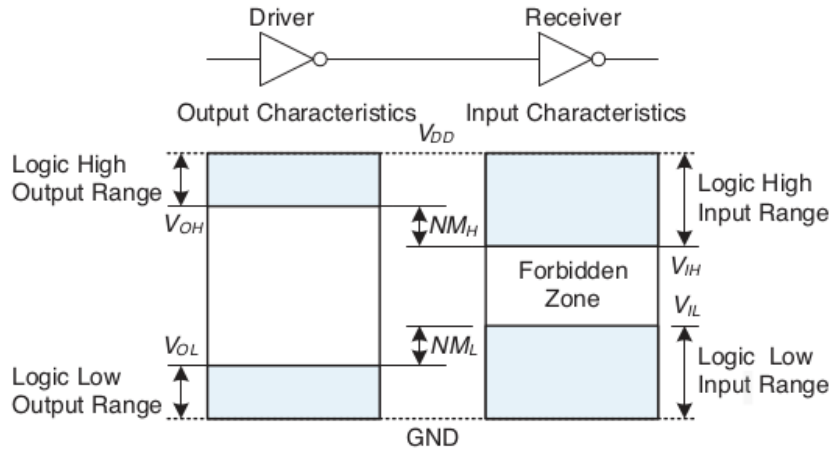

**Definition 3** (Supply Voltage ( $V_{DD}/V_{CC}/V_{SS}$ )).


**Definition 4** (Ground Voltage ( $V_{GND}$ )).

**Definition 5** (Input high ( $V_{IH}$ ) and Input Low ( $V_{IL}$ ) of a gate).

**Definition 6** (Output high ( $V_{OH}$ ) and Output low ( $V_{OL}$ ) of gate).

**Definition 7** (Positive logic and Negative logic).

**Definition 8** (Noise margins ( $NM_L$  and  $NM_H$ ) of a channel).

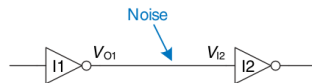

**Example 2.**

If  $V_{DD} = 5V$ ,  $V_{IL} = 1.35V$ ,  $V_{IH} = 3.15V$ ,  $V_{OL} = 0.33V$  and  $V_{OH} = 3.84V$  for both the “inverters”, then what are the low and high noise margins? Can the circuit tolerate 1V of noise at the channel?


## 4 Semiconductors and Doping

Not in syllabus but good to know

Elements recognized as metalloids V•T•E


	13	14	15	16	17
2	B Boron	C Carbon	N Nitrogen	O Oxygen	F Fluorine
3	Al Aluminium	Si Silicon	P Phosphorus	S Sulfur	Cl Chlorine
4	Ga Gallium	Ge Germanium	As Arsenic	Se Selenium	Br Bromine
5	In Indium	Sn Tin	Sb Antimony	Te Tellurium	I Iodine
6	Tl Thallium	Pb Lead	Bi Bismuth	Po Polonium	At Astatine

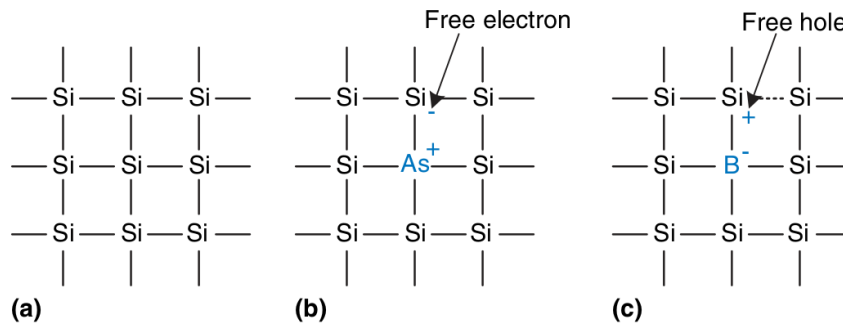Commonly recognized (86–99%): B, Si, Ge, As, Sb, Te  
 Irregularly recognized (40–49%): Po, At  
 Less commonly recognized (24%): Se  
 Rarely recognized (8–10%): C, Al  
 (All other elements cited in less than 6% of sources)  
 Arbitrary metal-nonmetal dividing line: between Be and B, Al and Si, Ge and As, Sb and Te, Po and At




## 5 MOSFET: Metal Oxide Field Effect Transistors

Not in syllabus but good to know

 

(a) nMOS


(b) pMOS

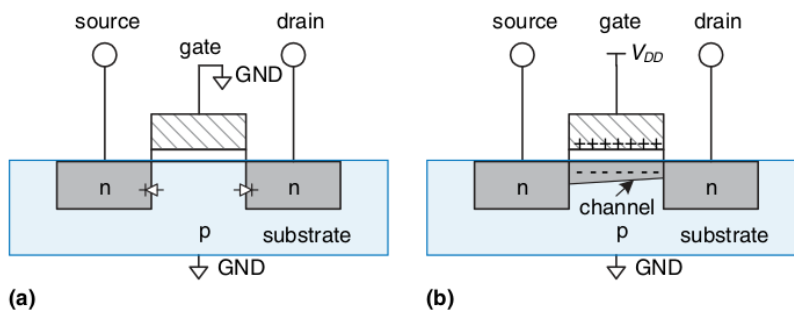

(a)



(b)

## 6 DC Transfer characteristic

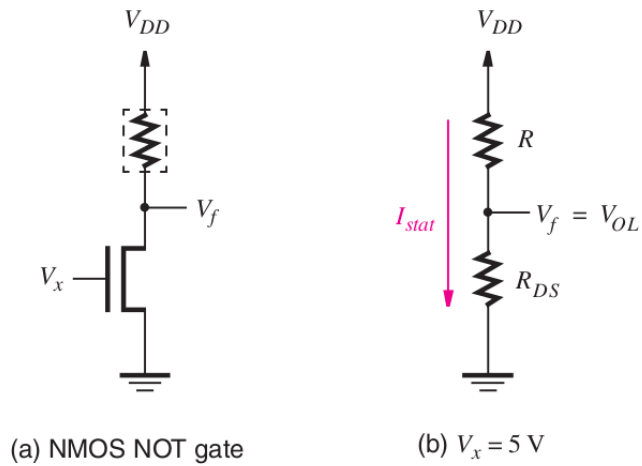


(a) NMOS NOT gate

(b)  $V_x = 5\text{ V}$

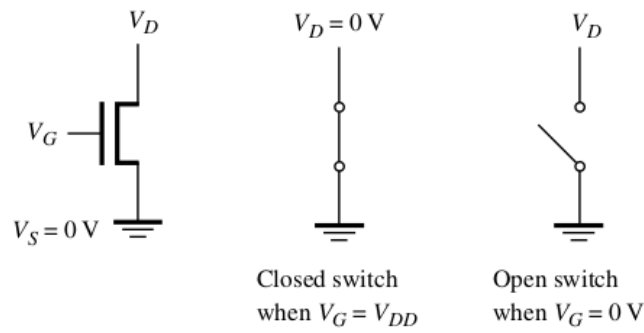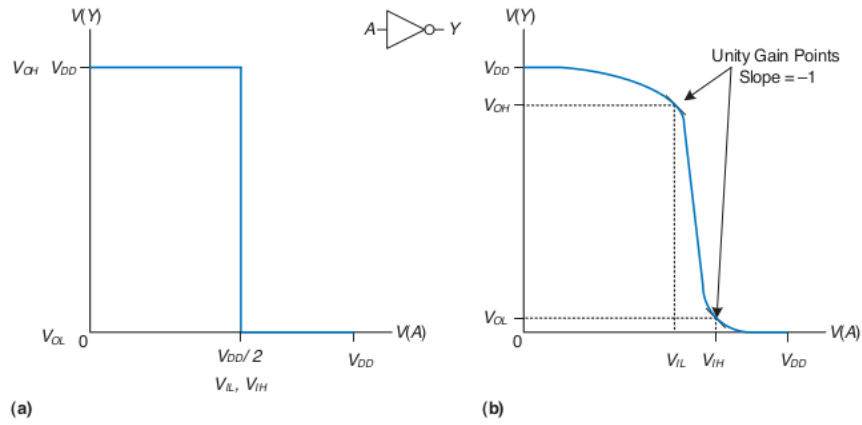

(a) NMOS transistor

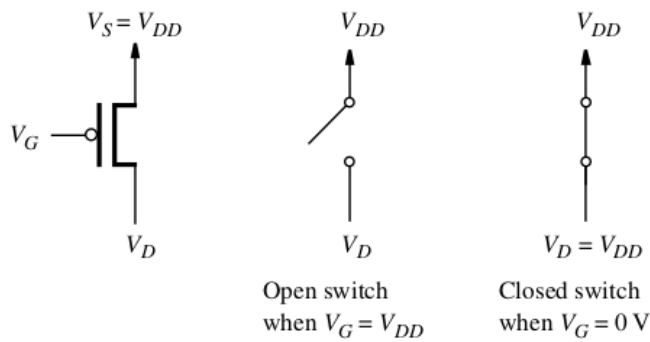

(b) PMOS transistor

**Example 3.** Draw a NOT gate using nMOS transistors.



**Example 4.** Draw a NOT gate using pMOS transistors.

**Remark 1.** nMOS transistors pass 0's well (output between 0 and  $V_{DD} - V_t$ ). pMOS transistors pass 1's well (output between  $V_t$  and  $V_{DD}$ ).

**Example 5.** Draw CMOS NOT Gate.

**Example 6.** Draw a two input CMOS NAND Gate


**Definition 9** (Negative logic).

**Example 7.** Analyze the above circuit under negative logic.


**Example 8.** Draw a three input NAND using CMOS.

**Example 9.** Draw a three input NOR using CMOS.

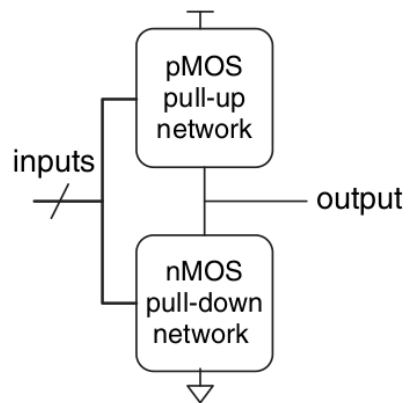**Example 10.** Draw a two input AND gate using CMOS.



## 6.1 Gates with floating output

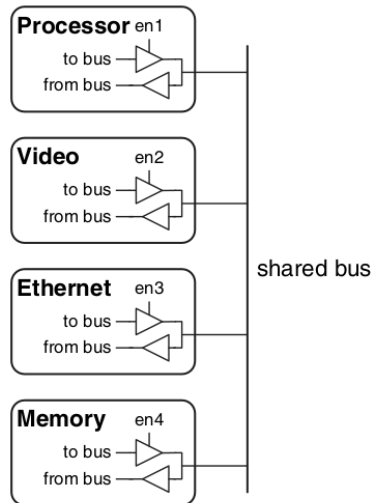

**Definition 10** (Transmission gate). *Draw a schematic of transmission gate and truth table for transmission gate. What is its commonly used symbol?*

**Definition 11** (Tristate buffer). *What is tristate buffer? Draw its symbol and truth table? Where is it used?*

**Example 11.** *Draw a Multiplexer using transmission gates.*

**Example 12.** *Draw a Multiplexer using tristate buffers.*

**Definition 12** (Totem-pole). *Draw a Push-pull (or Totem-pole) output NAND gate using CMOS. Can you connect this gate to a shared bus?*

**Definition 13** (Tristate). *Draw a Tristate output NAND gate using CMOS with an output enable (OE) input. Can you connect this gate to a shared bus?*

**Definition 14** (Open-collector). *Draw a open-collector output NAND gate. Can you connect this gate to a shared bus?*

## 7 Verilog truth tables

Table 11-11—Bitwise binary AND operator

&	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x

Table 11-12—Bitwise binary OR operator

	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

## References

- [1] Brown Stephen and Vranesic Zvonko. *Fundamentals of digital Logic with Verilog design*. McGraw Hill, 2022.