

MUX/DEC Sequential logic design

Vikas Dhiman for ECE275


December 1, 2023

1 Objectives

1. Design combinational circuits using multiplexers and decoders


2 Design combinational circuit using multiplexers [1, Section 2.8.1]

2.1 Review: 2to1 Multiplexer (MUX)

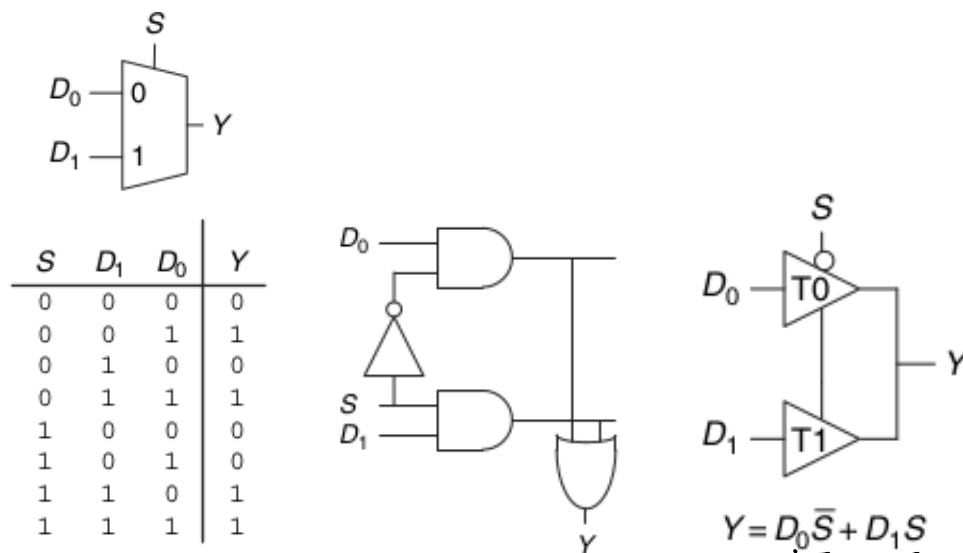

 2.2 Wider multiplexers

Draw the symbol for a 4:1 MUX, an 8:1 MUX and a $2^N : 1$ MUX and write corresponding Boolean expressions.




$$m_5 \quad m_4$$

$$A\bar{B}C + A\bar{B}\bar{C}$$

uses 4:1 MUX + gate

 Example 1. Design a circuit for $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$ using a 8:1 MUX.





$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$

$$m_5 \quad m_4$$

	A	B	C	Y
$Y = D_0$	0	0	0	1
$Y = D_1$	0	0	1	0
	0	1	0	0
	0	1	1	1
	1	0	0	1
	1	0	1	0
	1	1	0	0
$Y = D_7$	1	1	1	0



Remark 1. A $2^N : 1$ MUX can be used to program any N -input logic function.

Example 2. Design a circuit for $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$ using a 4:1 MUX and NOT gates only.

  


Remark 2. A $2^{N-1} : 1$ MUX can be used to program any N -input logic function, if we use literals on the input side.

  Example 3. Design a circuit for $Y = \bar{A}C + \bar{A}B + B\bar{D}$ using a 8:1 MUX and NOT gates only. Also design using 4:1 MUX and other gates. fewest gates.



3 Encoders and Decoders

 Example 4. Draw the symbol and the truth table for 2:4 decoder. Also write the logic expressions.



I_1	I_0	EN	O_3	O_2	O_1	O_0
*	*	0	0	0	0	0
0	0	1	0	0	0	1
0	1	1	0	0	1	0
1	0	1	0	1	0	0
1	1	1	1	0	0	0


$$O_0 = EN \cdot \bar{I}_1 \bar{I}_0$$

$$O_1 = EN \cdot \bar{I}_1 I_0$$

$$O_2 = EN \cdot I_1 \bar{I}_0$$


$$O_3 = EN \cdot I_1 I_0$$

 Example 5. Draw the symbol and the truth table for 3:8 decoder, 4:16 decoder and $N : 2^N$ decoder. Also write the logic expressions.




I_2	I_1	I_0	EN	O_7	O_6	...	O_1	O_0
*	*	*	0	0	0	...	0	0
0	0	0	1	0	0	...	0	1
 
$$O_5 = EN \cdot I_2 \bar{I}_1 \bar{I}_0$$




 
$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\cdot 0 + A\cdot\bar{B}\cdot 1$$





$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

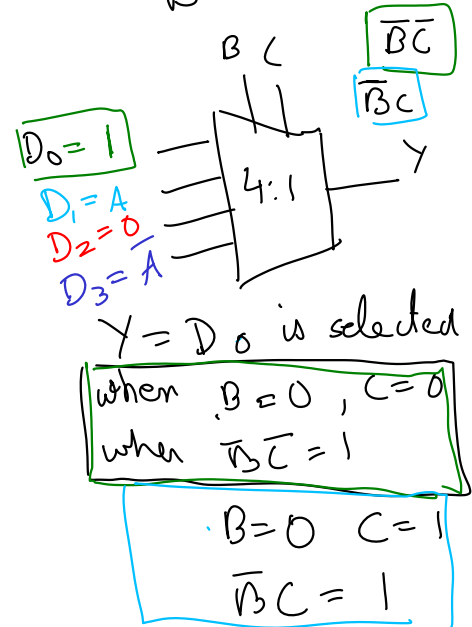 

$$Y = \bar{A}C + \bar{A}B + B\bar{D}$$

using 4:1 MUX + gates

  

\bar{Y} $AB=00$ then $Y=I_0$


$$I_0 = C$$

\bar{Y} $AB=00$ then $Y=I_0=C$

$$I_1 = 1$$

$$I_2 = 0$$


$$I_3 = \bar{D}$$

 


$$Y = A\bar{B} + \bar{A}B$$

$$Y = A \oplus B$$

Example 6. Design a circuit for a XOR gate using a 2:4 decoder and an OR gate.

 


 Example 7. Design a circuit for $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$ using a 3:8 decoder and an OR gate.



3.1 (Priority) Encoders

 Example 8. Draw symbol and truth table for a 4:2 priority encoder.




← Most significant bits
← higher priority

I_3	I_2	I_1	I_0	O_1	O_0	EN
0	0	0	0	0	0	0
0	0	0	1	0	0	1
0	0	1	*	0	1	1
0	1	*	*	1	0	1
1	*	*	*	1	1	1

$O_1 = I_3 + I_2$

 Example 9. Draw symbol and truth table for a 8:3 priority encoder.



I_7	I_6	I_5	I_4	I_3	I_2	I_1	I_0	O_2	O_1	O_0	EN
0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	0	0	1	*	0	0	0	1
0	0	0	0	1	*	*	*	0	0	1	1
0	0	0	1	*	*	*	*	0	1	0	1
0	0	1	*	*	*	*	*	0	1	1	1
0	1	*	*	*	*	*	*	1	0	0	1
1	*	*	*	*	*	*	*	1	1	1	1

8 rows

I_3	I_2	I_1	I_0
0	0	0	0
0	0	1	1
0	1	1	1
1	1	1	1

$O_1 = I_3 + I_2$

References

- [1] Sarah L Harris and David Harris. *Digital design and computer architecture*. Morgan Kaufmann, 2022.

FAN-IN and FAN-OUT

FAN-IN is the maximum number of inputs that you can connect to a gate

FAN-OUT is the max. number of gates that you can connect

to the output of a gate

$$FAN-IN = 4$$



$$FAN-OUT = 5$$

